

Chapter 17

9. (a) $V = V_1 + V_2 + V_3 = 1.5 \text{ V} + 1.5 \text{ V} + 1.5 \text{ V} = \boxed{4.5 \text{ V}}$. (b) $V = V_1 = V_2 = V_3 = \boxed{1.5 \text{ V}}$.

11. (a) $V = V_1 + V_2 + V_3 = 2(6.0 \text{ V}) + 12 \text{ V} = \boxed{24 \text{ V}}$.

(b) The $\boxed{\text{two } 6.0\text{-V in series, together in parallel with the } 12\text{-V}}$.

19. $I = \frac{q}{t} = \frac{30 \text{ C}}{120 \text{ s}} = \boxed{0.25 \text{ A}}$.

$\boxed{32}$. This is because the $\boxed{\text{resistance is low and the current is high at turn-on}}$. Once the lamp is hot, its resistance increases and current decreases, so there is less chance of burning out.

35. (a) $V = IR = (1.9 \text{ A})(6.0 \Omega) = \boxed{11.4 \text{ V}}$.

(b) $\varepsilon = V + Ir$, $r = \frac{\varepsilon - V}{I} = \frac{12 \text{ V} - 11.4 \text{ V}}{1.9 \text{ A}} = \boxed{0.32 \Omega}$.

$\boxed{38}$. $I = \frac{V}{R} = \frac{12 \text{ V}}{15 \Omega} = \boxed{0.80 \text{ A}}$.

41. $R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} = \frac{(1.70 \times 10^{-8} \Omega \cdot \text{m})(0.60 \text{ m})}{\pi (0.05 \times 10^{-2} \text{ m})^2} = \boxed{1.3 \times 10^{-2} \Omega}$.

47. (a) $\Delta R = R_0 \alpha \Delta T = (25 \text{ m}\Omega)(6.80 \times 10^{-3} \text{ C}^{-1})(27 \text{ C}^\circ) = \boxed{4.6 \text{ m}\Omega}$.

(b) $I_0 = \frac{V}{R_0}$ and $I = \frac{V}{R}$. $\frac{I}{I_0} = \frac{R_0}{R} = \frac{25 \text{ m}\Omega}{(25 + 4.6) \text{ m}\Omega} = 0.845$. $I = (0.845)I_0 = (0.845)(10.0 \text{ mA}) = \boxed{8.5 \text{ mA}}$.

68. (a) $I = \frac{V}{R} = \frac{1.50 \text{ V}}{2.50 \Omega} = \boxed{0.600 \text{ A}}$.

(b) $q = It = (0.600 \text{ A})(6.00 \text{ h})(3600 \text{ s/h}) = \boxed{1.30 \times 10^4 \text{ C}}$.

(c) $E = qV = (1.30 \times 10^4 \text{ C})(1.50 \text{ V}) = \boxed{1.94 \times 10^4 \text{ J}}$.

Alternate method: $E = pt = I^2 Rt = (0.600 \text{ A})^2(2.50 \Omega)(6.00 \text{ h})(3600 \text{ s/h}) = 1.94 \times 10^4 \text{ J}$.